



University of British Columbia  
ELEC291/ELEC292

## Lab 3: 555 timer and Capacitance Meter

Dr. Jesús Calviño-Fraga P.Eng.  
Department of Electrical and Computer Engineering, UBC  
Office: KAIS 3024  
E-mail: [jesusc@ece.ubc.ca](mailto:jesusc@ece.ubc.ca)  
Phone: (604)-827-5387

January 28, 2022

© Jesús Calviño-Fraga, 2009-2022. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## Objectives

- Lab 3 requirements.
- The 555 timer.
- Read capacitors.
- Measure Frequency
- Measure Period
- 32-bit unsigned integer arithmetic.

ELEC291/ELEC292 Lab 3

© Jesús Calviño-Fraga, 2009-2022. Not to be copied, used, or revised without explicit written permission from the copyright owner.

2

# Lab Requirements


- 555 Timer:
  - a) Test the 555 timer as an A-stable oscillator.
  - b) Use a 555 timer to measure capacitance:
    - Range: 1nF to 1μF. No decimal places required.
    - Display value using LCD.
    - Program AT89LP51RC2 using assembly language.

ELEC291/ELEC292 Lab 3

© Jesús Calviño-Fraga, 2009-2022. Not to be copied, used, or revised without explicit written permission from the copyright owner.

3

## 555 Timer astable (oscillator)

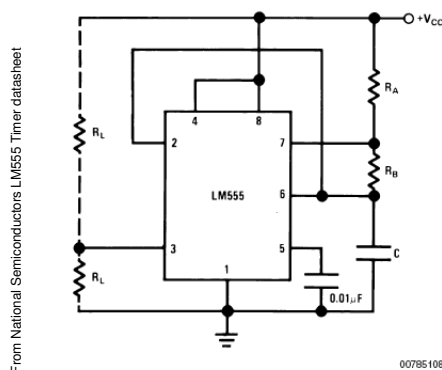

$$f = \frac{1}{T} = \frac{1.44}{(R_A + 2R_B)C}$$

FIGURE 4. Astable

ELEC291/ELEC292 Lab 3

© Jesús Calviño-Fraga, 2009-2022. Not to be copied, used, or revised without explicit written permission from the copyright owner.


4

# Information in BB2Scope Manual
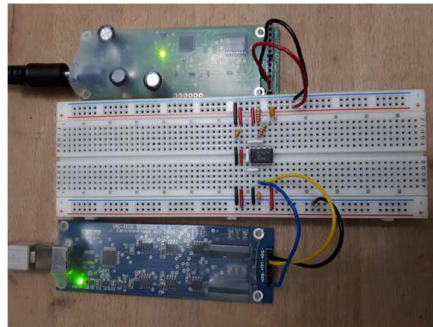
## 555 Timer A-stable Oscillator

The picture of the bread-boarded circuit below shows a 555 timer configured as an A-stable oscillator ( $R_1=R_2=2.2k\Omega$ ;  $C=0.1\mu F$ ). The power for the 555 timer IC (approximately 5V) is obtained from the Gen2BB board +5V output. The schematic diagram of this circuit can be found here:


<https://ohmslawcalculator.com/555-astable-calculator>



© Jesús Calviño-Fraga, 2009-2022. Not to be copied, used, or revised without explicit written permission from the copyright owner.
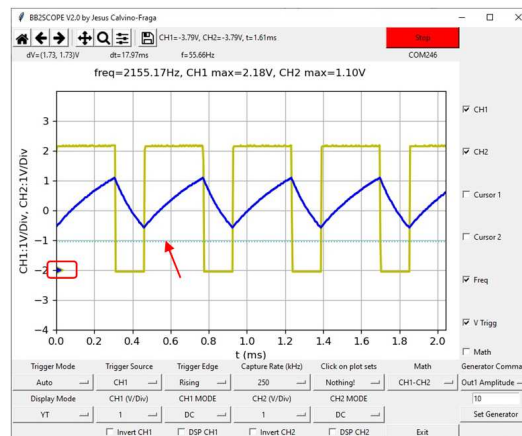
# Information in BB2Scope Manual

The figure below was obtained while the 555 timer A-stable oscillator was connected to BB2Scope board. CH1 shows the output of the timer (IC pin 3), while CH2 shows the voltage at the timing capacitor (IC pin 2).




ELEC291/ELEC292 Lab 3

© Jesús Calviño-Fraga, 2009-2022. Not to be copied, used, or revised without explicit written permission from the copyright owner.

<https://ohmslawcalculator.com/555-astable-calculator>

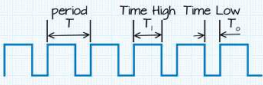**555 Astable Circuit Calculator**

The 555 timer is capable of being used in astable and monostable circuits. In an astable circuit, the output voltage alternates between VCC and 0 volts on a continual basis.




By selecting values for R<sub>1</sub>, R<sub>2</sub>, and C we can determine the period/frequency and the duty cycle.

The period is the length of time it takes for the on/off cycle to repeat itself, whilst the duty cycle is the percentage of time the output is on i.e.  $T_H/T$ .

In this type of circuit, the duty cycle can never be 50% or lower.

Capacitor (C)	47	microFarad (µF)
Resistance 1 (R <sub>1</sub> )	10	k10ohms (kΩ)
Resistance 2 (R <sub>2</sub> )	10	k10ohms (kΩ)

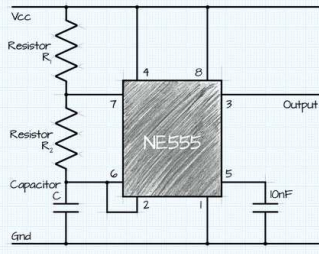


ELEC291/ELEC292 Lab 3

© Jesús Calviño-Fraga, 2009-2022. Not to be copied, used, or revised without explicit written permission from the copyright owner.

7

## Multisim 555 Timer Wizard

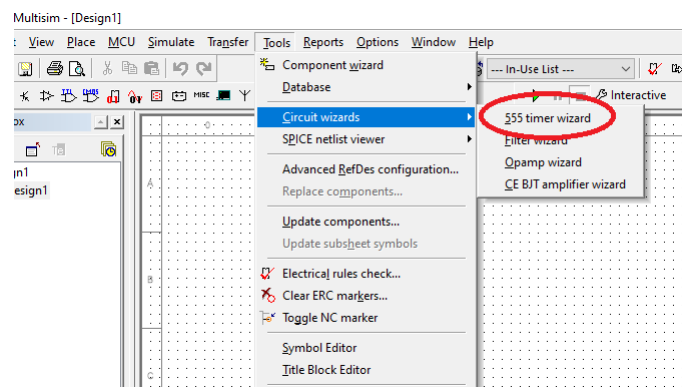


ELEC291/ELEC292 Lab 3

© Jesús Calviño-Fraga, 2009-2022. Not to be copied, used, or revised without explicit written permission from the copyright owner.

8

# Multisim 555 Timer Wizard

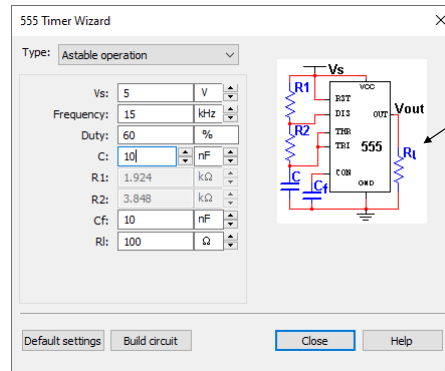

Don't put  $R_L$ !

ELEC291/ELEC292 Lab 3

© Jesús Calviño-Fraga, 2009-2022. Not to be copied, used, or revised without explicit written permission from the copyright owner.

9

## Capacitor Types

- Ceramic. Small values, small size, good price, good tolerance (lowest around  $\pm 1\%$ )
- Electrolytic. Large value, high tolerance ( $\pm 10\%$  minimum), don't age well, big size, very temperature sensitive.
- Tantalum. Large value, low voltage, small size, expensive, lowest tolerance around  $\pm 5\%$ .
- Mica. Best capacitors ever! Lowest tolerance around  $\pm 0.5\%$ . Very small values. VERY expensive, around 4\$ each!
- Polyester Film. Wide range values, inexpensive, good tolerance, price depends on tolerance and voltage rating
- Glass.


ELEC291/ELEC292 Lab 3

© Jesús Calviño-Fraga, 2009-2022. Not to be copied, used, or revised without explicit written permission from the copyright owner.

10
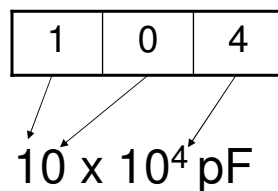
## How to read Capacitor Codes

- Large capacitors have their values printed on them, for example 10 $\mu$ F, 50V, 85C.
- Most small capacitors use a three number code system:



ELEC291/ELEC292 Lab 3

© Jesús Calviño-Fraga, 2009-2022. Not to be copied, used, or revised without explicit written permission from the copyright owner.

11

## How to read Capacitor Codes

- Tolerance is indicated by a letter after the value:

E	± 0.5%
F	± 1%
G	± 2%
H	± 3%
J	± 5%
K	± 10%
M	± 20%
N	± 30%
P	+100% , -0%
Z	+80%, -20%

If tolerance is not indicated assume it is 'Z': +80%, -20%.

ELEC291/ELEC292 Lab 3

© Jesús Calviño-Fraga, 2009-2022. Not to be copied, used, or revised without explicit written permission from the copyright owner.

12

# How to read Capacitor Codes

- Examples:
  - 103J
    - $10 \times 10^3 \pm 5\% = 0.01\mu\text{F} \pm 5\%$
  - 681
    - $68 \times 10^1 +80\%, -20\% = 680\text{pF} +80\%, -20\%$
  - 104Z
    - $10 \times 10^4 +80\%, -20\% = 0.1\mu\text{F} +80\%, -20\%$
  - 224M
    - $22 \times 10^4 \pm 20\% = 0.22\mu\text{F} \pm 20\%$
  - 473K
    - $47 \times 10^3 \pm 10\% = 47\text{nF} \pm 10\%$

ELEC291/ELEC292 Lab 3

© Jesús Calviño-Fraga, 2009-2022. Not to be copied, used, or revised without explicit written permission from the copyright owner.

13

# Using the Kit Multimeter to Measure Capacitance



Marking  
says: 103

ELEC291/ELEC292 Lab 3

© Jesús Calviño-Fraga, 2009-2022. Not to be copied, used, or revised without explicit written permission from the copyright owner.

14

## Using a Counter to Measure Frequency


- By definition “frequency” in Hz is the number of pulses in one second, so:
  - 1) Set up the counter to count pulses in one of the pins in the microcontroller.
  - 2) Reset the counter to zero.
  - 3) Enable the counter.
  - 4) Wait one second.
  - 5) Disable the counter. The counter register (THx, TLx) has the frequency in Hz!

ELEC291/ELEC292 Lab 3

© Jesús Calviño-Fraga, 2009-2022. Not to be copied, used, or revised without explicit written permission from the copyright owner.

15

## Using a Counter to Measure Frequency

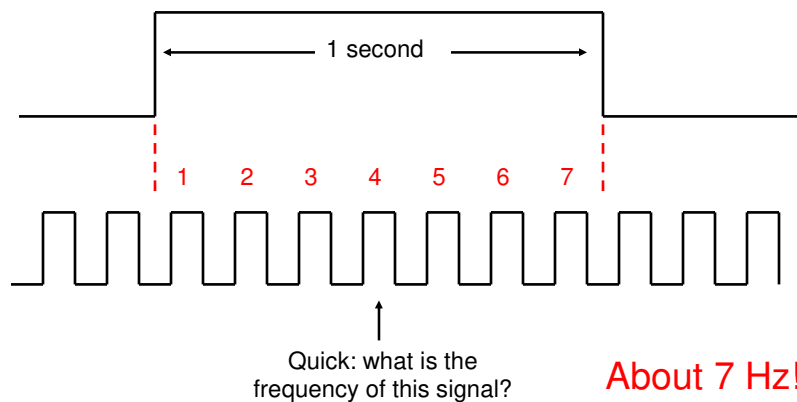

ELEC291/ELEC292 Lab 3

© Jesús Calviño-Fraga, 2009-2022. Not to be copied, used, or revised without explicit written permission from the copyright owner.

16



## Freq\_RC2.asm


- Available on Canvas

ELEC291/ELEC292 Lab 3

© Jesús Calviño-Fraga, 2009-2022. Not to be copied, used, or revised without explicit written permission from the copyright owner.

17
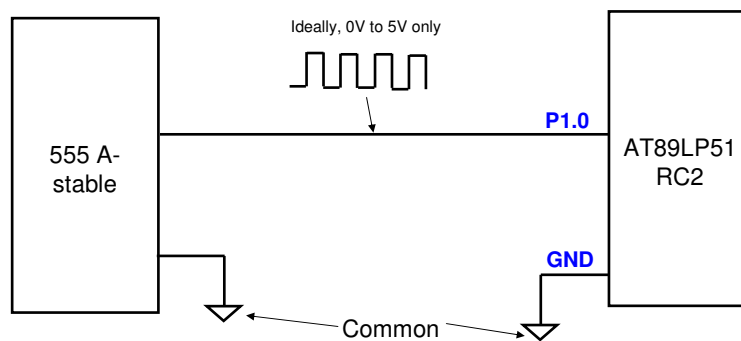
## Testing Freq\_RC2.asm with the 555 timer



ELEC291/ELEC292 Lab 3

© Jesús Calviño-Fraga, 2009-2022. Not to be copied, used, or revised without explicit written permission from the copyright owner.

18

## Measure Period Using a Timer in the 8051

- We can measure the period of a wave in integer numbers of the timer clock period. Some math may be required!
- Works quite well for slow signals.
- Measuring period is way faster than measuring frequency.

ELEC291/ELEC292 Lab 3

© Jesús Calviño-Fraga, 2009-2022. Not to be copied, used, or revised without explicit written permission from the copyright owner.

19

## Measure Period Using a Timer in the 8051


- To measure period we have to:
  - 1) Set up the timer.
  - 2) Connect the signal to be measured to any available pin. Also, set the pin as input.
  - 3) Reset the timer to zero.
  - 4) Wait for the input signal to transition from zero to one.
  - 5) Start the timer.
  - 6) Wait for the input signal to transition from zero to one.
  - 7) Stop the timer! The timer SFRs (THx, TLx) have the period in timer-input-period units!

ELEC291/ELEC292 Lab 3

© Jesús Calviño-Fraga, 2009-2022. Not to be copied, used, or revised without explicit written permission from the copyright owner.

20
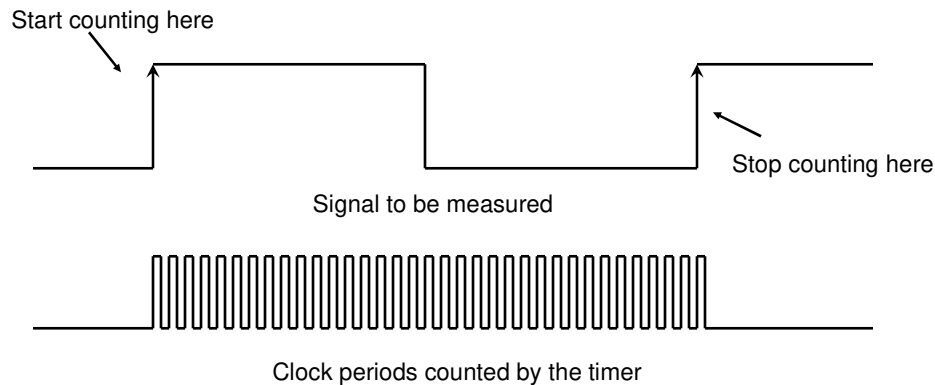
## Measure Period Using a Timer in the 8051



Signal period is about 35 timer periods. For a AT89LP51RC2 (@22.1184MHz), the period of the signal would be approximately  
 $T = (35/22.1184E6) = 1.582393\mu s$

ELEC291/ELEC292 Lab 3

21

© Jesús Calviño-Fraga, 2009-2022. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## 32-bit Arithmetic Library Math32

- **Math32.asm** has the following functions:
  - **Hex2bcd**: Converts the 32-bit binary number in 'x' to a 10-digit packed BCD in 'bcd' using the double-dabble algorithm. Largest BCD possible is 4,294,967,295.
  - **Bcd2hex**: Converts the 10-digit packed BCD in 'bcd' to a 32-bit binary number in 'x'. Largest hex number is 0xffffffff.
  - **add32**:  $x = x + y$
  - **sub32**:  $x = x - y$
  - **mul32**:  $x = x * y$
  - **div32**:  $x = x / y$
  - **x\_lt\_y**: mf=1 if  $x < y$  (mf is a bit)
  - **x\_gt\_y**: mf=1 if  $x > y$
  - **x\_eq\_y**: mf=1 if  $x = y$
  - **x\_gteq\_y**: mf=1 if  $x \geq y$
  - **x\_lteq\_y**: mf=1 if  $x \leq y$
  - **xchg\_xy**: exchange x and y
  - **copy\_xy**: copy x to y
- **Math32.asm** has the following macros:
  - **Load\_X** or **Load\_Y**: load x or y with a 32-bit constant

ELEC291/ELEC292 Lab 3

22

© Jesús Calviño-Fraga, 2009-2022. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## Math32 Test Program

- **Mathtest.asm** shows how to:
  - Define the x, y, bcd, and mf variables.
  - Include the math32 library in your program.
  - Use the Load\_X and Load\_X macros.
  - Convert a binary to BCD using bin2bcd and display it using the LCD.
  - Use the add32, sub32, mul32, and div32 functions.
  - Evaluate a formula using only integers.

ELEC291/ELEC292 Lab 3

© Jesús Calviño-Fraga, 2009-2022. Not to be copied, used, or revised without explicit written permission from the copyright owner.

23

## Warning: You are using integer arithmetic!

$$V_{out} = \frac{ADC}{(2^{10} - 1)} \times V_{REF} = \frac{ADC}{1023} \times 410$$

Formula we want to calculate

Suppose ADC=612, compute Vout

$$V_{out} = \frac{612}{1023} \times 410$$

Wrong!

$$V_{out} = (612 / 1023) \times 410 = (0) \times 410 = 0$$

$$V_{out} = (612 \times 410) / 1023 = (250920) / 1023 = 245$$

Right!

ELEC291/ELEC292 Lab 3

© Jesús Calviño-Fraga, 2009-2022. Not to be copied, used, or revised without explicit written permission from the copyright owner.

24

## Final Remarks

- Lab 3 is an excellent starting point for project 1!
- Copy 16-bit timer count to 32-bit x:

```
mov x+0, TL2
```

```
mov x+1, TH2
```

```
mov x+2, #0 ; load high bits with zero
```

```
mov x+3, #0 ; load high bits with zero
```

ELEC291/ELEC292 Lab 3

© Jesús Calviño-Fraga, 2009-2022. Not to be copied, used, or revised without explicit written permission from the copyright owner.

25